

**Homework 2**  
**Due Friday, September 20<sup>th</sup> at 11:00pm via CMS**

Notes:

- (1) Submit your solution in a single PDF file named HW2.pdf
  - (2) Put your name and NetID on the top of the first page
  - (3) Show how you arrived at your answers
- 

**Problem 1.**

For a 1-bit 2-to-1 mux:

- (a) Draw the truth table.
- (b) Draw a Karnaugh Map with the zeros from the truth table.
- (c) Derive a minimum product-of-sums Boolean expression from the K-Map.
- (d) Implement (c) using only NOT and NOR gates.


**Problem 2.**

Implement the truth table below using an 8-to-1 mux and no inverters.

<b>A</b>	<b>B</b>	<b>C</b>	<b>D</b>	<b>F</b>
0	0	0	0	0
0	0	0	1	1
0	0	1	0	0
0	0	1	1	1
0	1	0	0	1
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

**Problem 3.**

Determine the Boolean expression for  $F$  in SOP form (you don't need to minimize).

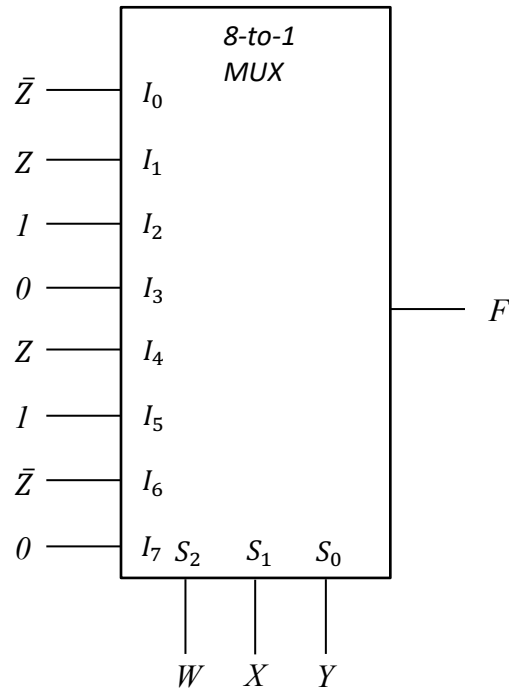

**Problem 4.**

For the following logic function draw a truth table and minimize the function using a Karnaugh Map. Implement the minimized function using NOT, AND, and OR gates. Then implement the function from the truth table using a 3-to-8 decoder and 2-input NAND and/or NOR gates.

$$F = \sum_{XYZ} (0,2,4,5)$$